
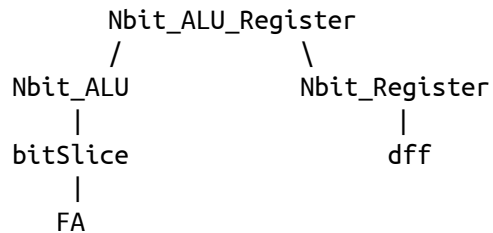


Leonardo Mattos Martins
 U25267206
 Lab 4 Writeup


Code hierarchy:

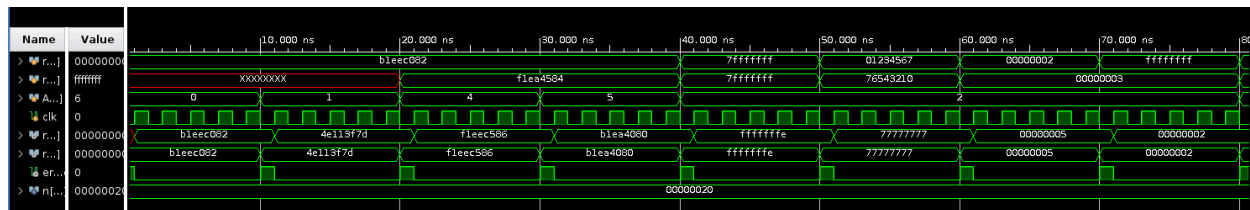

Waveform screenshots: testbench for Nbit_ALU_Register (Nbit_ALU_tb)
 MOV, NOT, OR, AND, and ADD operations



SUB and SLT operations

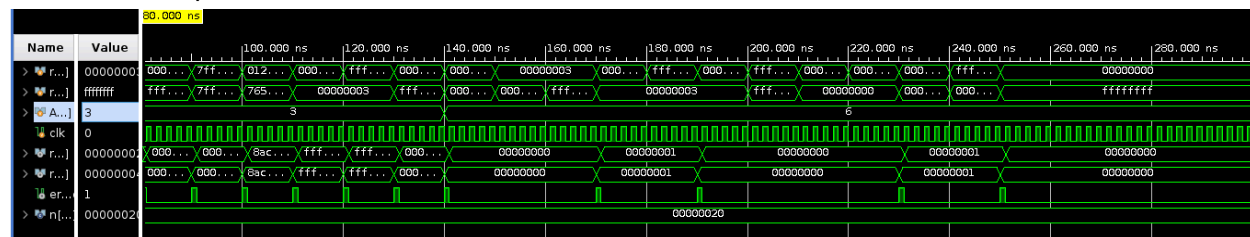

Module Descriptions:

FA
 Full Adder

bitSlice
 A 1-bit ALU which performs MOV, NOT, AND, OR, ADD, SUB, and SLT operations on 2 1-bit inputs and selected the appropriate output based on an operation code ALUop using a 3-bit MUX

Nbit_ALU
 Generates n many bitSlice blocks which work together to perform the same operations on any given amount of bits based on the given parameter

dff
 D flip-flop; catches input and stores in a register

Nbit_Register

Generates n many dffs to store any given amount of bits into a register, based on the given parameter

Nbit_ALU_Register

Combines Nbit_ALU and Nbit_Register to perform operation on 2 inputs of a given size and store the result in a register.